

Encoder

(Address and Branch Control Logic)

T-Table

	$I_7$	$I_6$	$I_5$	$I_4$	$I_3$	$I_2$	$I_1$	$I_0$
0	0	0	0	0	0	0	0	1
1	0	0	0	0	0	0	1	0
2	0	0	0	0	0	1	0	0
3	0	0	0	0	1	0	0	0
4	0	0	0	1	0	0	0	0
5	0	0	1	0	0	0	0	0
6	0	1	0	0	0	0	0	0
7	1	0	0	0	0	0	0	0

	$A_2$	$A_1$	$A_0$
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

Address lines

ONE switch on at a time!

Von Neumann Architecture

$$A_2 = I_4 + I_5 + I_6 + I_7$$

$$A_1 = I_2 + I_3 + I_6 + I_7$$

$$A_0 = I_1 + I_3 + I_5 + I_7$$

OR Gate  $I_n \rightarrow A_n$

47 → 0

By Inversion.

Address lines → Row terms

$A_2$   $A_1$   $A_0$  arrange

0 0 1

0 1 0

0 1 1

1 0 0

1 0 1

1 1 0

1 1 1

$$A_2' A_1' A_0' = y_0$$

$$A_2' A_1' A_0 = y_1$$

$$A_2' A_1 A_0' = y_2$$

$$A_2' A_1 A_0 = y_3$$

$$A_2 A_1' A_0' = y_4$$

$$A_2 A_1' A_0 = y_5$$

$$A_2 A_1 A_0' = y_6$$

$$A_2 A_1 A_0 = y_7$$

Exactly 2/8 LED's light for any given Address.

Build "Matrix" (i.e., unit/Hex:2.) through Horizontal/Vertical arrangement. Instruction arrangement.



Matrix is  $(8 \times 4)$   
(Horiz. Unit.)

$(y_0 \rightarrow y_7)$  Horizontally

$(Q_3 \rightarrow Q_0)$  Vertically

$Q_T = 1$   
for  $4^{th}$  cym.

	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$S_2 S_1 S_0$ output
$y_0$	0	0	0	0	000 $CH_0$
$y_1$	0	0	1	0	001 $CH_1$
$y_2$	0	1	0	0	010 $CH_2$
$y_3$	0	1	1	0	011 $CH_3$
$y_4$	1	0	0	0	100 $CH_4$
$y_5$	1	0	1	0	101 $CH_5$
$y_6$	1	1	0	0	110 $CH_6$
$y_7$	1	1	1	0	111 $CH_7$

iff  $\exists$  connection between  
 $y_n$  and  $Q_k$ ;

then,  $y_n = 1, Q_k = 0$ .

iff  $\nexists$  connection,  
then,  $Q_k = 1$ .

By Changing which intersections are Connected,

I can change the Rom's "program" [i.e., the control words  
H' outputs for each  
Address (AI)].

Thus, ~~prog~~ Programmable in the sense of  
Rewiring or Rearranging the Jumper wires to define NEW  
MICRO-INSTRUCTIONS.

Bus Enable =  $y \cdot T$ .